

Module 4:FLIP-FLOP

Quote of the day

“Never think you are nothing, never think you are everything, but think you are something and achieve anything”.

— Albert Einstein




Sequential and combinational circuits

- A digital circuit whose output depends on only applied input is combinational circuit.
- Digital circuits studied until now are combinational circuits
- A digital circuit whose output not only depends on applied input but also depends on the present state of output is Sequential circuit.
- Sequential circuit has memory.
- Flip-flop is a basic element of sequential circuit.

FLIP-FLOP

 
- A basic sequential circuit is a flip-flop
- Flip-flop has two stable states of complementary output values



Simple flip-flop.

NOR Gate Latch \ SR Flip-flop

 - SR (set-reset) flip-flop based on two nor gates.
- If $R=0, S=0$ then output of both NOR gates depend on other inputs ,i.e Q and \bar{Q}
- Assume $Q=0$ and $\bar{Q}=1$ initially
- Observe that out put will not change




An *SR* flip-flop can be implemented by cross coupling two NOR gates.

SR-FLIP-FLOP			
R	S	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

NOR Gate Latch \ SR Flip-flop

 - SR (set-reset) flip-flop based on two nor gates.
- If $R=0, S=0$ then output of both NOR gates depend on other inputs ,i.e Q and \bar{Q}
- Assume $Q=1$ and $\bar{Q}=0$ initially
- Observe that out put will not change




An *SR* flip-flop can be implemented by cross coupling two NOR gates.

SR-FLIP-FLOP			
R	S	Q	\bar{Q}
0	0	Last state	
0	1		
1	0		
1	1		

NOR Gate Latch \ SR Flip-flop

 - SR (set-reset) flip-flop based on two nor gates.
- If $R=0, S=1$ then output of Gate 2 becomes one, i.e. $\bar{Q} = 0$ and output of gate 1 which depends on \bar{Q} becomes 1.
- Observe that out put set to one whatever may be previous state of O/P.




An SR flip-flop can be implemented by cross coupling two NOR gates.

SR-FLIP-FLOP			
R	S	Q	\bar{Q}
0	0	Last state	
0	1	1	0
1	0		
1	1		

NOR Gate Latch \ SR Flip-flop

 - SR (set-reset) flip-flop based on two nor gates.
- If $R=1, S=0$ then output of Gate 1 becomes zero, i.e $Q= 0$ and output of gate 2 which depends on Q becomes 1.
- Observe that out put reset to zero whatever may be previous state of O/P.




An SR flip-flop can be implemented by cross coupling two NOR gates.

SR-FLIP-FLOP			
R	S	Q	\bar{Q}
0	0	Last state	
0	1	1	0
1	0	0	1
1	1		

NOR Gate Latch \ SR Flip-flop

 - SR (set-reset) flip-flop based on two nor gates.
- If $R=1, S=1$ then output of both Gates becomes zero, i.e. $Q=0$ and $\bar{Q}=0$.
- This is not allowed state of Flip Flop.
- Is Illegal state or Forbidden state of Flip-flop




An SR flip-flop can be implemented by cross coupling two NOR gates.

SR-FLIP-FLOP			
R	S	Q	\bar{Q}
0	0	Last state	
0	1	1	0
1	0	0	1
1	1	Illegal	

NAND Gate Latch \ $\bar{S}\bar{R}$ Flip-flop

 - $\bar{S}\bar{R}$ (set-reset) flip-flop based on two nor gates.
- If $\bar{R}=0, \bar{S}=0$ then output of both Gates becomes one, i.e. $Q=1$ and $\bar{Q}=1$.
- This is not allowed state of Flip Flop.
- Is Illegal state or Forbidden state of Flip-flop




A flip-flop implemented with NAND gates.

$\bar{S}\bar{R}$ -FLIP-FLOP			
\bar{R}	\bar{S}	Q	\bar{Q}
0	0	Illegal	
0	1		
1	0		
1	1		

NAND Gate Latch \ $\bar{S}\bar{R}$ Flip-flop

$\bar{S}\bar{R}$ (set-reset) flip-flop based on two nor gates.

 - If $\bar{R}=0, \bar{S}=1$ then output of Gate-2 becomes one, i.e $\bar{Q}=1$ and output of gate 1 which depends on \bar{Q} becomes 0.
- Observe that out put reset to zero whatever may be previous state of O/P.




A flip-flop implemented with NAND gates.

$\bar{S}\bar{R}$ -FLIP-FLOP			
\bar{R}	\bar{S}	Q	\bar{Q}
0	0	Illegal	
0	1	0	1
1	0		
1	1		

NAND Gate Latch \ $\bar{S}\bar{R}$ Flip-flop

 - $\bar{S}\bar{R}$ (set-reset) flip-flop based on two nor gates.
- If $\bar{R}=1, \bar{S}=0$ then output of Gate-1 becomes one, i.e $Q=1$ and output of gate 2 which depends on Q becomes 0.
- Observe that out put set to one whatever may be previous state of O/P.




A flip-flop implemented with NAND gates.

$\bar{S}\bar{R}$ -FLIP-FLOP			
\bar{R}	\bar{S}	Q	\bar{Q}
0	0	Illegal	
0	1	0	1
1	0	1	0
1	1		

NAND Gate Latch \ $\bar{S}\bar{R}$ Flip-flop

 - $\bar{S}\bar{R}$ (set-reset) flip-flop based on two nor gates.
- If $\bar{R}=1, \bar{S}=1$ then output of both NOR gates depend on other inputs ,i.e Q and \bar{Q} .
- Assume $Q=1$ and $\bar{Q}=0$ initially.
- Observe that out put will not change.




A flip-flop implemented with NAND gates.

$\bar{S}\bar{R}$ -FLIP-FLOP			
\bar{R}	\bar{S}	Q	\bar{Q}
0	0	Illegal	
0	1	0	1
1	0	1	0
1	1		

NAND Gate Latch \ $\bar{S}\bar{R}$ Flip-flop

 - $\bar{S}\bar{R}$ (set-reset) flip-flop based on two nor gates.
- If $\bar{R}=1, \bar{S}=1$ then output of both NOR gates depend on other inputs ,i.e Q and \bar{Q} .
- Assume $Q=0$ and $\bar{Q}=1$ initially.
- Observe that out put will not change.



A flip-flop implemented with NAND gates.

SR-FLIP-FLOP			
\bar{R}	\bar{S}	Q	\bar{Q}
0	0	Illegal	
0	1	0	1
1	0	1	0
1	1	Last state	

Truth table


\bar{R}	\bar{S}	R	S	Q	\bar{Q}
0	0	1	1	Illegal	
0	1	1	0	0	1
1	0	0	1	1	0
1	1	0	0	Last state	

SR-FLIP-FLOP

R	S	Q	\bar{Q}	Output(Q)
0	0	Last state		Last state
0	1	1	0	Set
1	0	0	1	Reset
1	1	Illegal		Illegal

Flip-Flop

 - The previous slides described you the NAND/NOR Gate Latch.
- You observed that a latch using NAND is referred as $\bar{S}\bar{R}$ latch.




A flip-flop implemented with NAND gates.

SR-FLIP-FLOP			
\bar{R}	\bar{S}	Q	\bar{Q}
0	0	Illegal	
0	1	0	1
1	0	1	0
1	1	Last states	

- To obtain SR latch using NAND gates, we are suppose to add two NOT gates implemented using NAND gates at the terminal of these inputs $\bar{S}\bar{R}$.


SR latch using NAND gates Flip-flop

 

Truth table

R	S	\bar{R}	\bar{S}	Q^+	\bar{Q}^+
0	0	1	1	Last state	
0	1	1	0	1	0
1	0	0	1	0	1
1	1	0	0	Illegal	


Logical Symbol

 

Gated Flip-Flops

- In the latches observed till now output responds immediately to the changes in input.
- In many digital systems it is required that the circuit responds only at some prescribed time, decided by another input called the enable or clock input.
- A Flip-Flop which immediately responds to the changes of input in spite of enable or clock input is referred as latch.
- Some flip-flops responds to the changes of input during the edges of the clock inputs.


Gated Flip-Flops

 

(a) Circuit diagram

R	S	C	Q_n
0	0	\times	Q_{n-1}
0	1	1	1
1	0	1	0
1	1	1	Not allowed
\times	\times	0	Q_{n-1}

(b) Truth table

 


(b) Circuit symbol

A clocked SR flip-flop.

- The latch will disable with $C=0$ and continue the last state. The output is said to be latched.
- It will enable with $C=1$ and function as normal SR F/F.
- Q_n is present state of output, Q_{n-1} last state of output state

Gated Latch-Clocked RS Flip-flop

 


A clocked *SR* flip-flop.

R	S	$Enable$	Q_n
0	0	×	Q_{n-1}
0	1	1	1
1	0	1	0
1	1	1	Not allowed
×	×	0	Q_{n-1}

Truth table

Logical Symbol

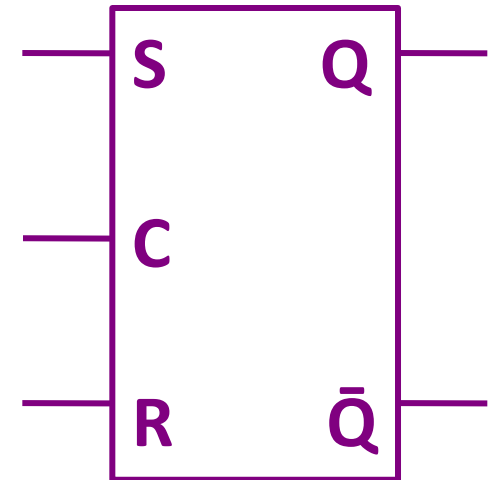

Input output waveform

